

Digital System Design

ESE 218 – Section: L03

**Bonus Lab: Analog to Digital Converter**

May 5<sup>th</sup>, 2018

Roni Das : 108378223

The **Objective** of this lab is to Design Master controller based on IceStick FPGA with SPI-compatible protocol for communication with 10-bit ADC MCP3001. Datasheet for MCP3001 was thoroughly revised and requirements noted down.

MCP 3001 Requirments .


Clock : 13 periods

$\overline{CS}$  : Active Low.

known,

$$LSB \text{ size} = \frac{V_{REF}}{1024}$$
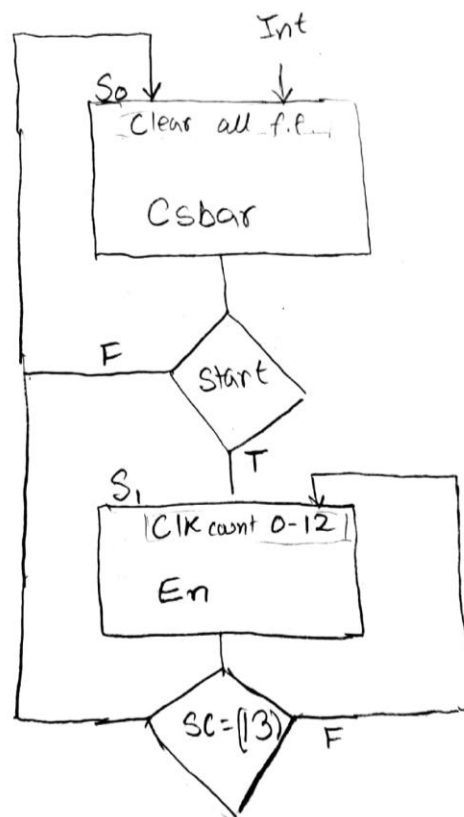
$$\text{Digital output code} = \frac{1024 \times V_{IN}}{V_{REF}}$$




ASM chart for controller

Figure 1: Controller design.
 
### **Approaches taken to reach objective as follows:**

Design a control unit in Hardware descriptive language which will communicate with MCP3001 via programmable FPGA. From Datasheet of MCP3001 it was noted that it requires 13 clock periods to calculate after CSbar has been pulled down. Our goal is to provide these 13 clock periods to MCP3001 with the help of a counter. ADC provides, MSB first, at falling edge starting from 3<sup>rd</sup> Clock pulse. Data Out from ADC is then fed into a 10-bit Serial In Parallel Out Shift Register to observe ADC values.

SPI Master consists of Controller, a 10-bit SIPO SR and a 4-bit Up counter. System starts upon initialization = 1; Before initialization states of the flip flops are unknown. With Int= 1, CSbar goes High clearing all flip flops incident to system. CSbar is also applied to ADC, putting it into high impedance mode. System idles at this state (S0), until Starts = 1. With St=1; CSbar goes down and Enable set to High. With Enable =1, Counter starts counting from 0 as clock pulses are provided to ADC and other components of the system. With SC= 1 at 13; CSbar goes High and count stops, En = 0; setting the state back to S0. Visualization of these processes can be derived from Schematics of the circuit and its simulated waveforms (presented below). Note that Clock for ADC is function of both Enable and Clock. In this lab, Clock to ADC is named MCLK. Same Clock periods, MCLK is also given to SIPO as it does not need more to push out data. One key difference of the operation of ADC (provides Serial in for SIPO), and SIPO SR is that One same Clock period they work on different edges of the clock; ADC provides data on Falling edge of the clock while SIPO takes in on the Rising edge of the Clock. Therefore, as soon as the data is available at ADC output, immediate rising edge of next MCLK data is processed through SIPO.



State diagram for controller.

Present state variable	present state	INPUTS			Next state	Outputs	
$S_0/S_1$	$G_0$	$\overline{St}$	$\overline{Int}$	$\overline{SC}$	$G_0^*$	$\overline{En}$	$\overline{Csbars}$
?	?	X	0	X	X	X	X
$S_0$	0	X	1	X	0	0	1
$S_0$	0	0	X	X	0	0	1
$S_0$	0	1	X	X	1	0	1
$S_1$	1	X	X	0	1	1	0
$S_1$	1	X	X	1	0	1	0

$$\textcircled{1} \quad G_0^* = \overline{G_0} St + G_0 \overline{SC}$$


$$\textcircled{2} \quad \overline{En} = G_0 \overline{SC} + G_0 SC$$

$$\textcircled{3} \quad \overline{Csbars} = \overline{G_0} \overline{Int} + \overline{G_0} \overline{St} + \overline{G_0} St$$

Figure 2: State Diagram and Table for Controller.

Since, it's a one variable state, only a single D- flip flop is required to cycle through the states.

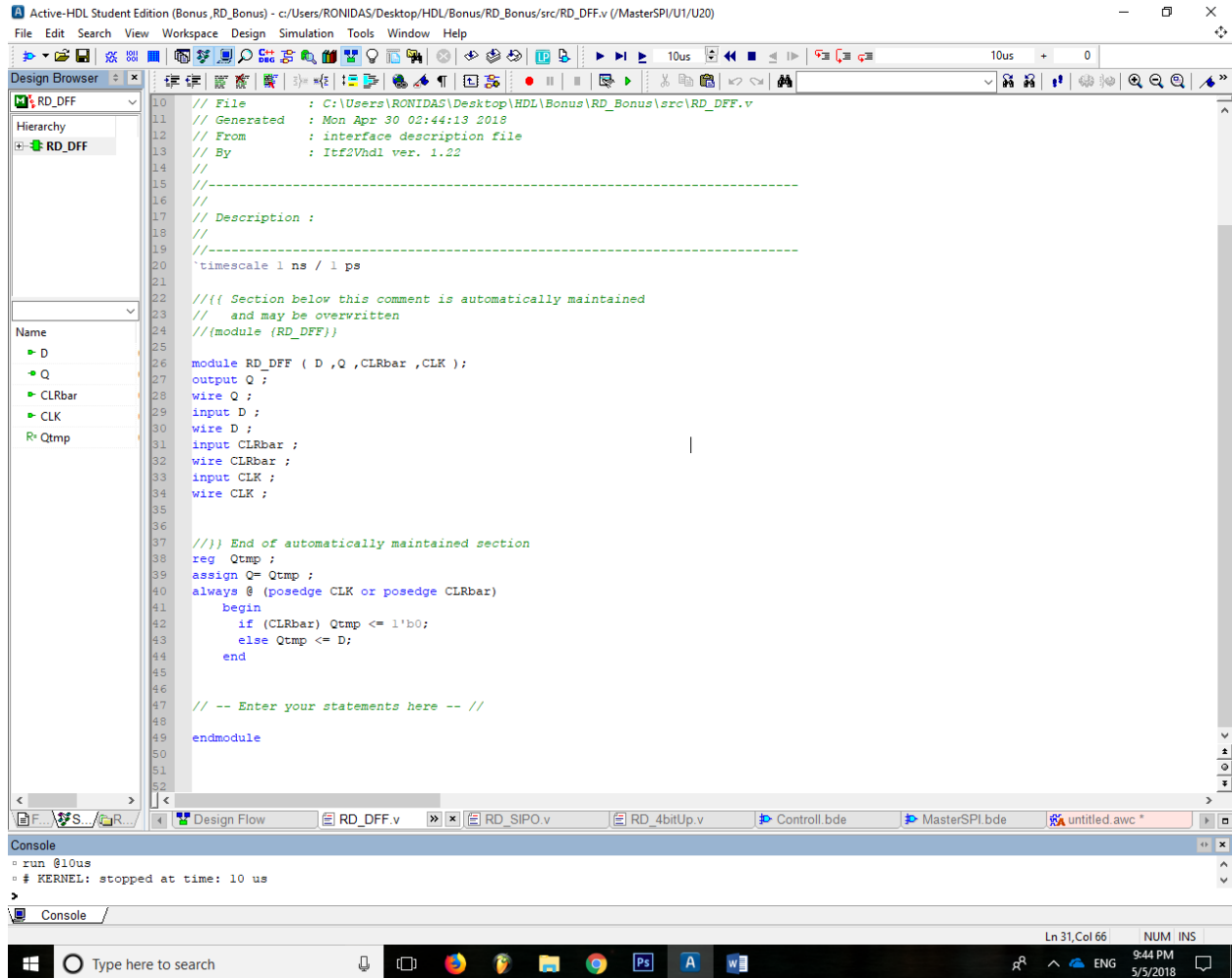For convenience of error free operation, all Verilog models and Schematics from HDL was verified in Simulation mode. Following presents those results



The screenshot displays the Active-HDL Student Edition interface. The main window shows the Verilog source code for a D-Flip Flop model named RD\_DFF.v. The code includes a module definition with inputs D, CLRbar, and CLK, and an output Q. It uses a reg Qtmp and an always block to implement the flip-flop logic. The simulation is run at 10ns, and the console output shows the simulation stopping at 10ns.

```
10 // File : C:\Users\RONIDAS\Desktop\HDL\Bonus\RD_Bonus\src\RD_DFF.v
11 // Generated : Mon Apr 30 02:44:13 2018
12 // From : interface description file
13 // By : Itf2Vhdl ver. 1.22
14 //
15 //-----
16 //
17 // Description :
18 //
19 //-----
20 `timescale 1 ns / 1 ps
21
22 //({ Section below this comment is automatically maintained
23 // and may be overwritten
24 //(module {RD_DFF})
25
26 module RD_DFF ( D ,Q ,CLRbar ,CLK );
27 output Q ;
28 wire Q ;
29 input D ;
30 wire D ;
31 input CLRbar ;
32 wire CLRbar ;
33 input CLK ;
34 wire CLK ;
35
36
37 //({ End of automatically maintained section
38 reg Qtmp ;
39 assign Q= Qtmp ;
40 always @ (posedge CLK or posedge CLRbar)
41 begin
42 if (CLRbar) Qtmp <= 1'b0;
43 else Qtmp <= D;
44 end
45
46 // -- Enter your statements here -- //
47
48 endmodule
49
50
51
52
```

Console Output:

```
run @10ns
# KERNEL: stopped at time: 10 ns
```

Figure 3: Verilog model for D-Flip Flop.

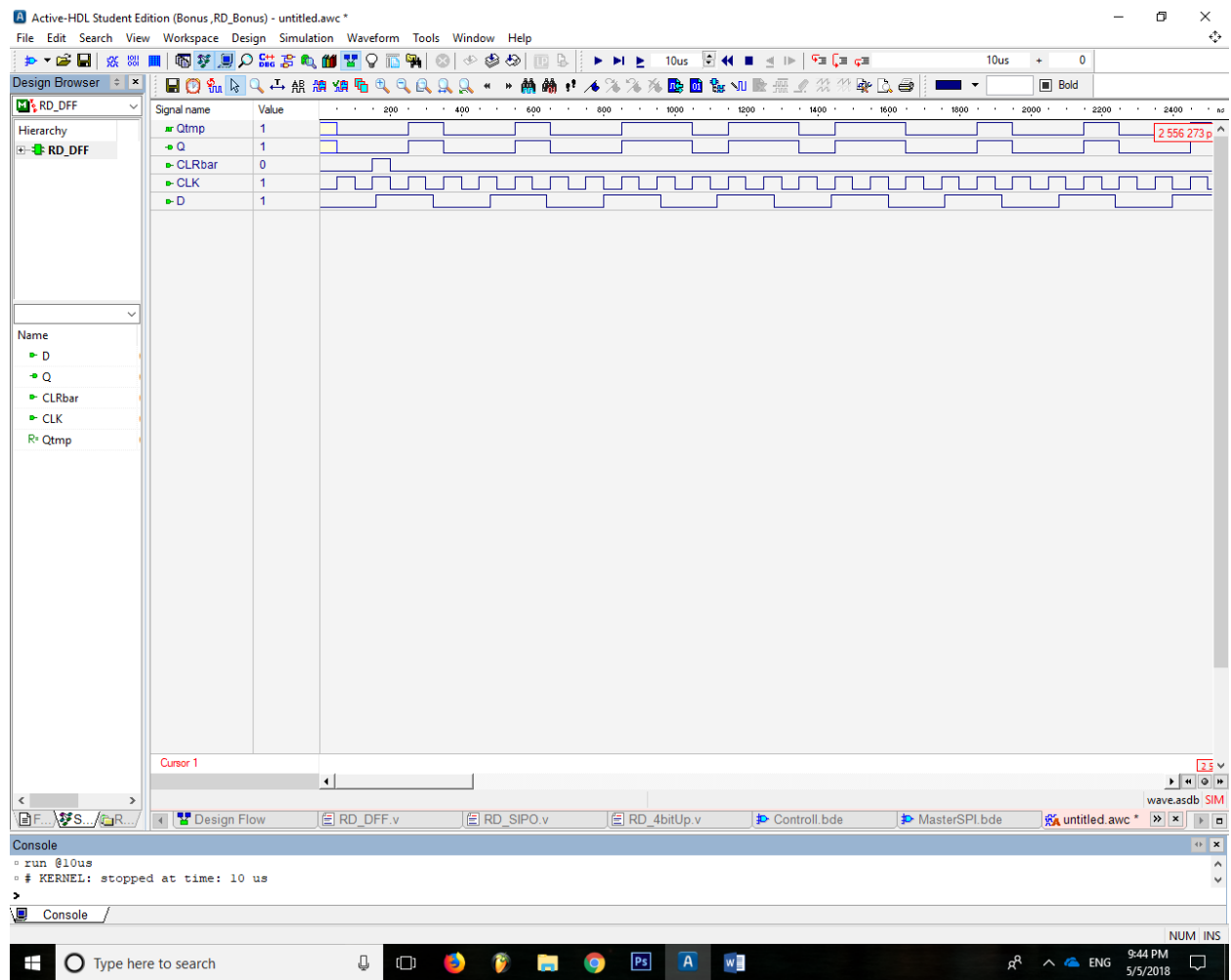


Figure 4: Operation of D-Flip Flop Verified.

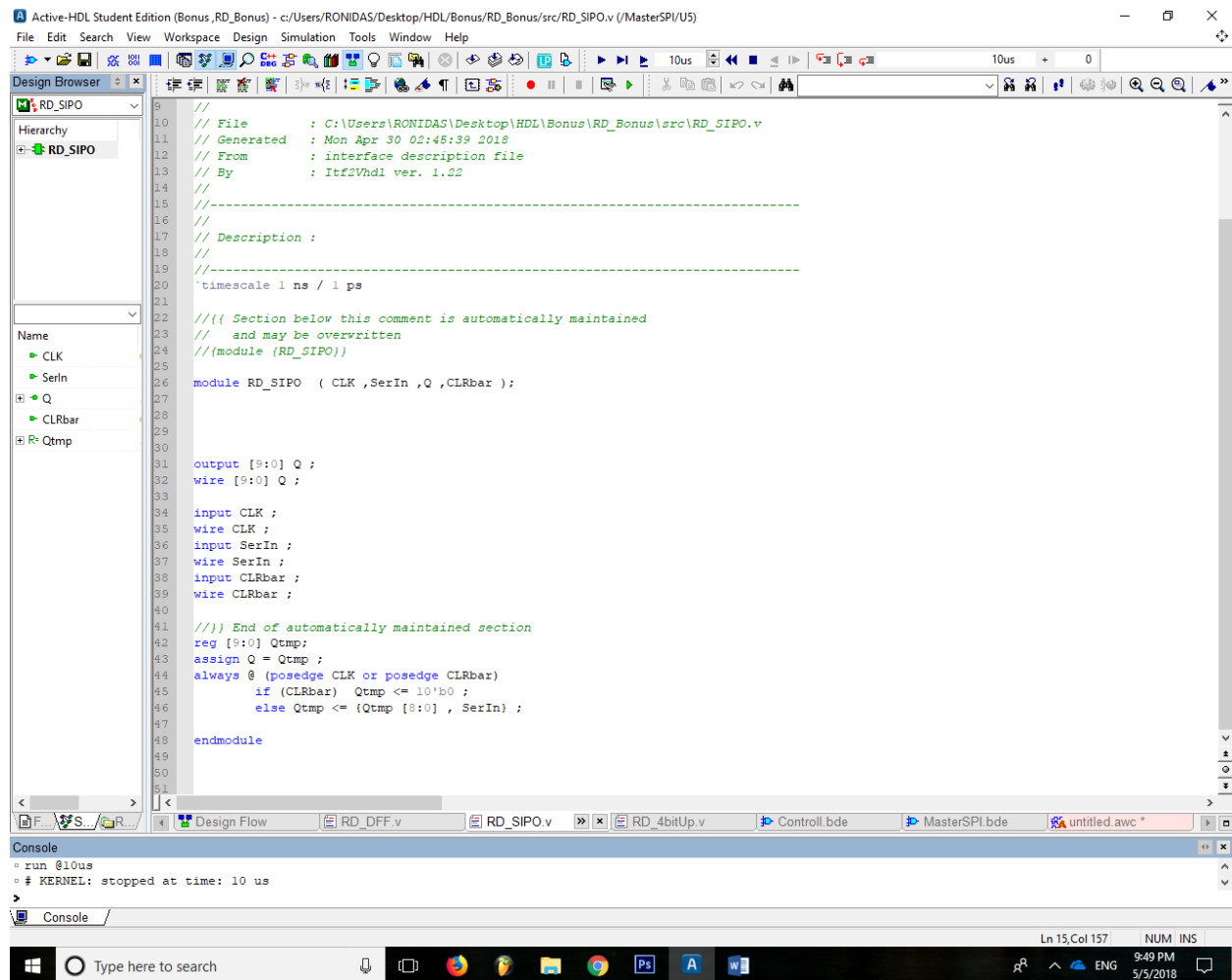


Figure 5: Verilog model for Serial in Parallel Out Shift Register.

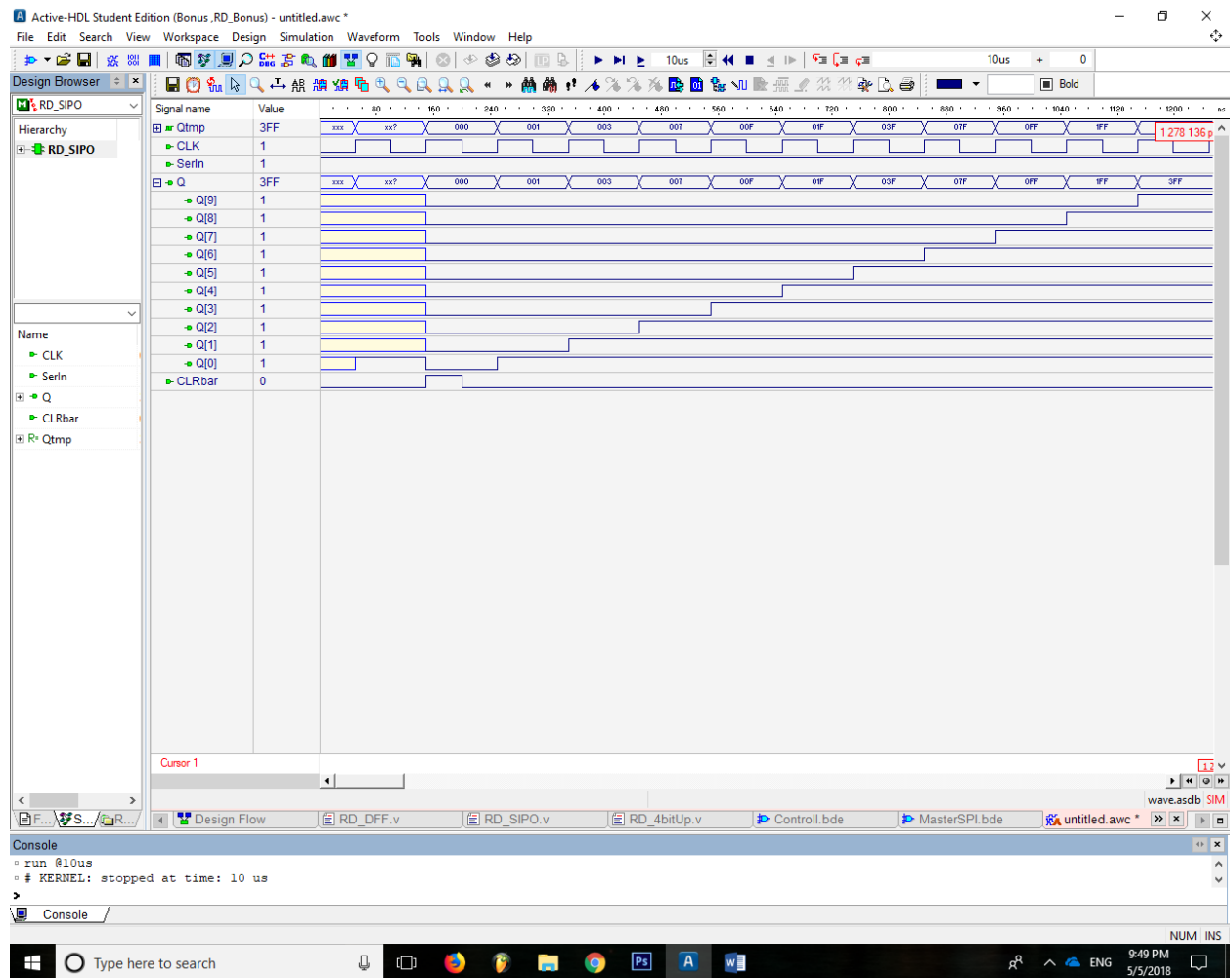


Figure 6 : Operation of SIPO SR verified.



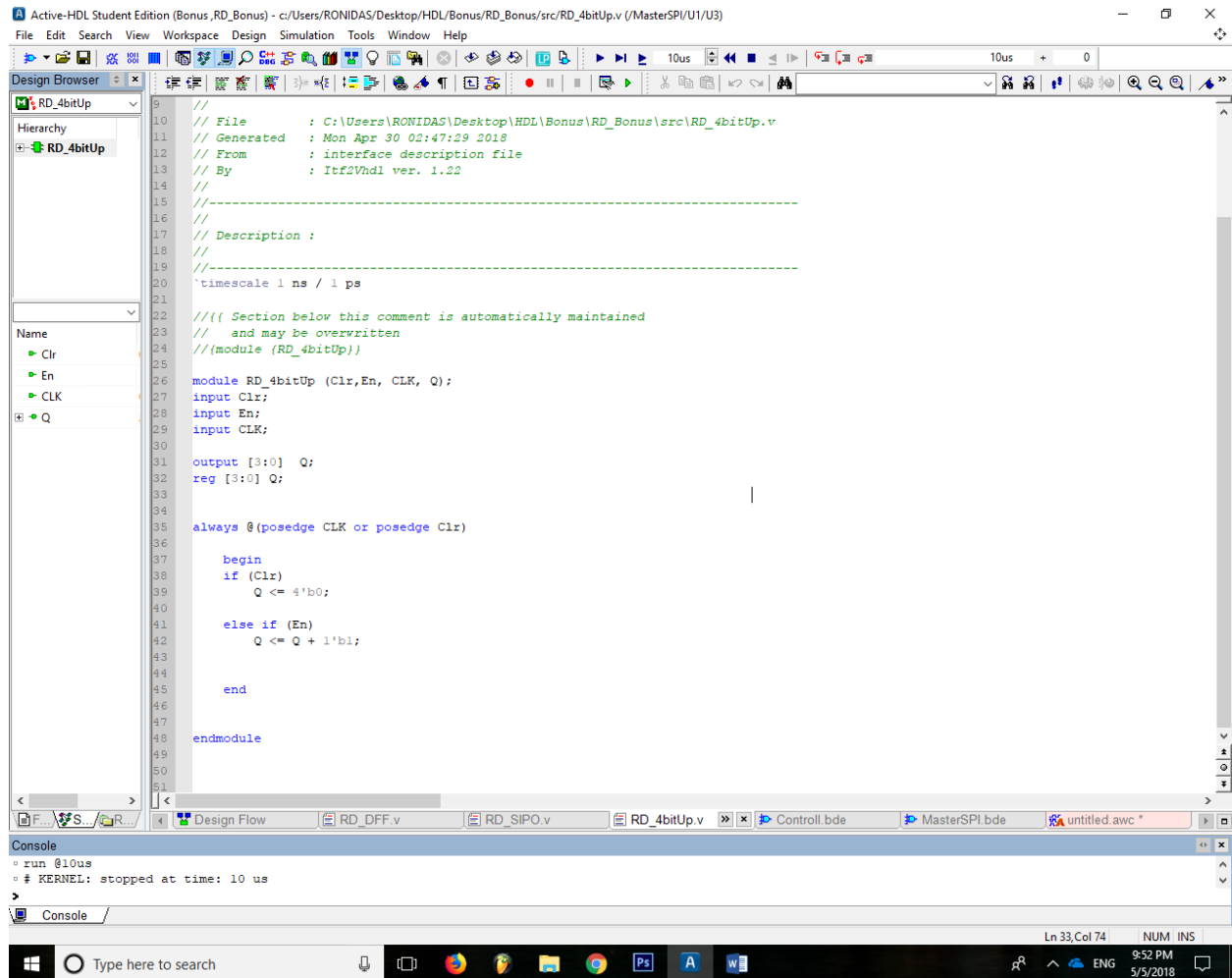


Figure 7: Verilog model for 4-bit Up Counter.

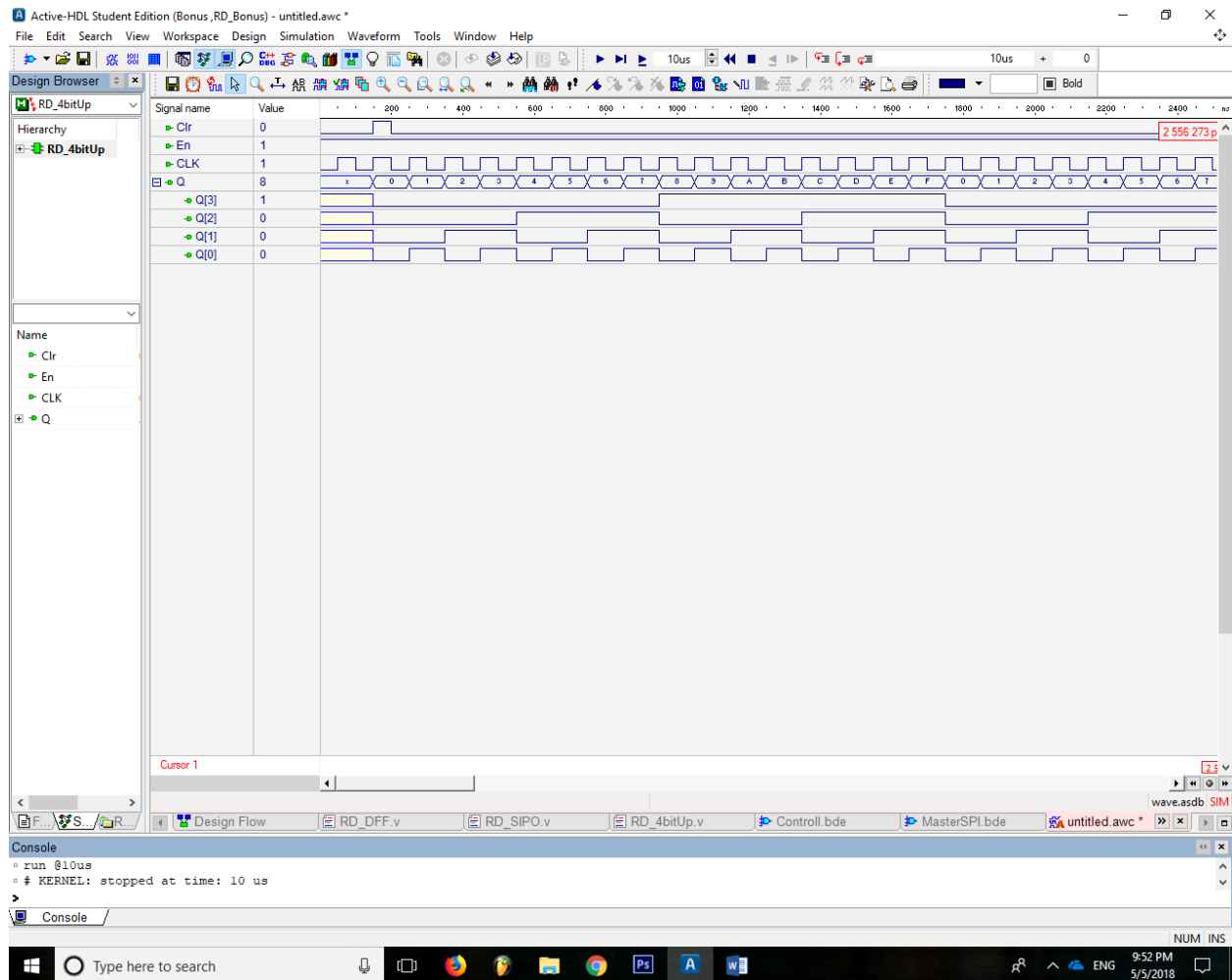


Figure 8 : Operation of 4-bit Up Counter verified using simulation.



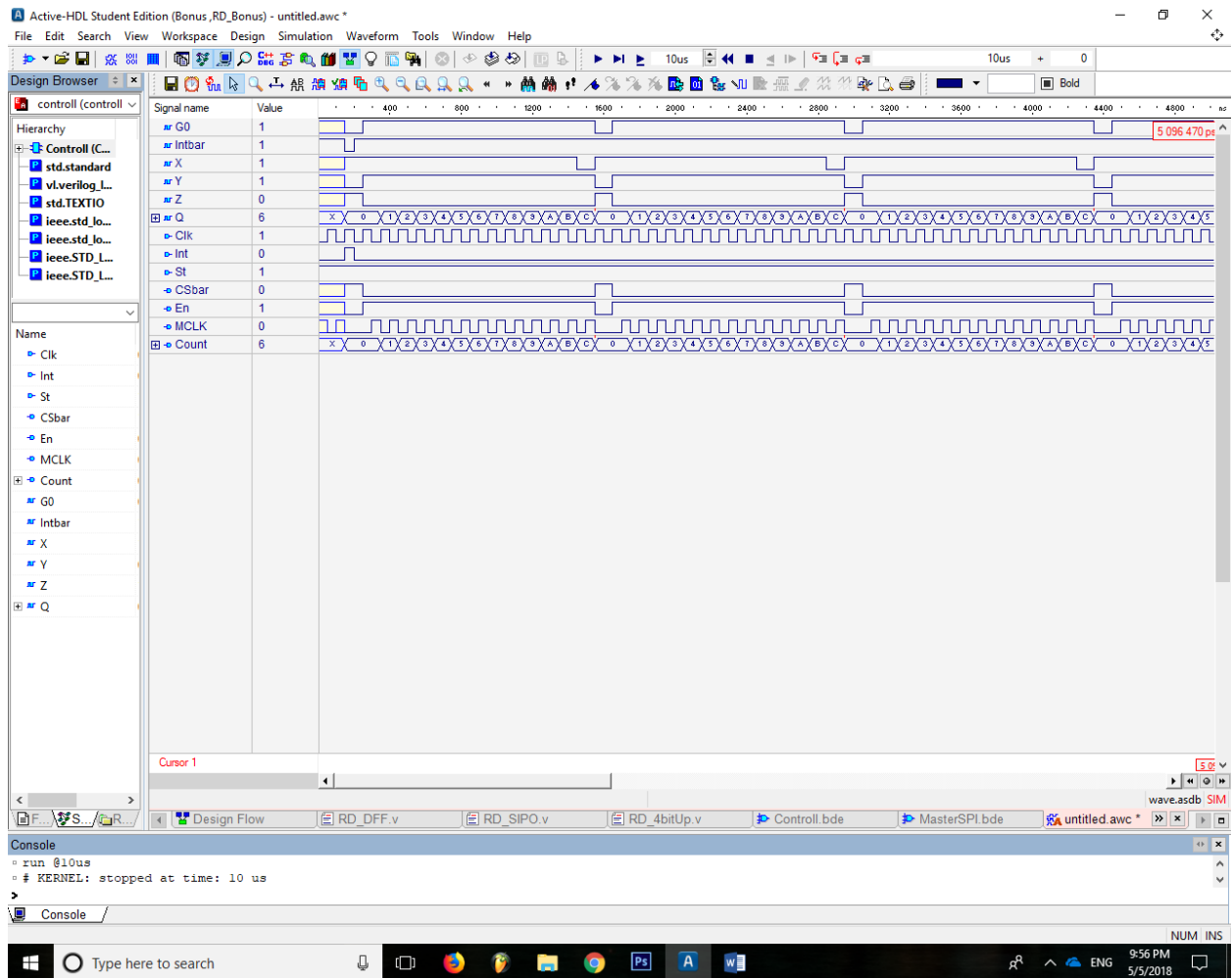


Figure 10 : Operation of Controller and Counter verified from simulation.

From waveforms above, we can denote that MCLK = 13 clock periods. On the last falling edge of MCLK CSbar changes to 1 ; Waveforms of CSbar and MCLK was compared against MCP3001 datasheet and verified.

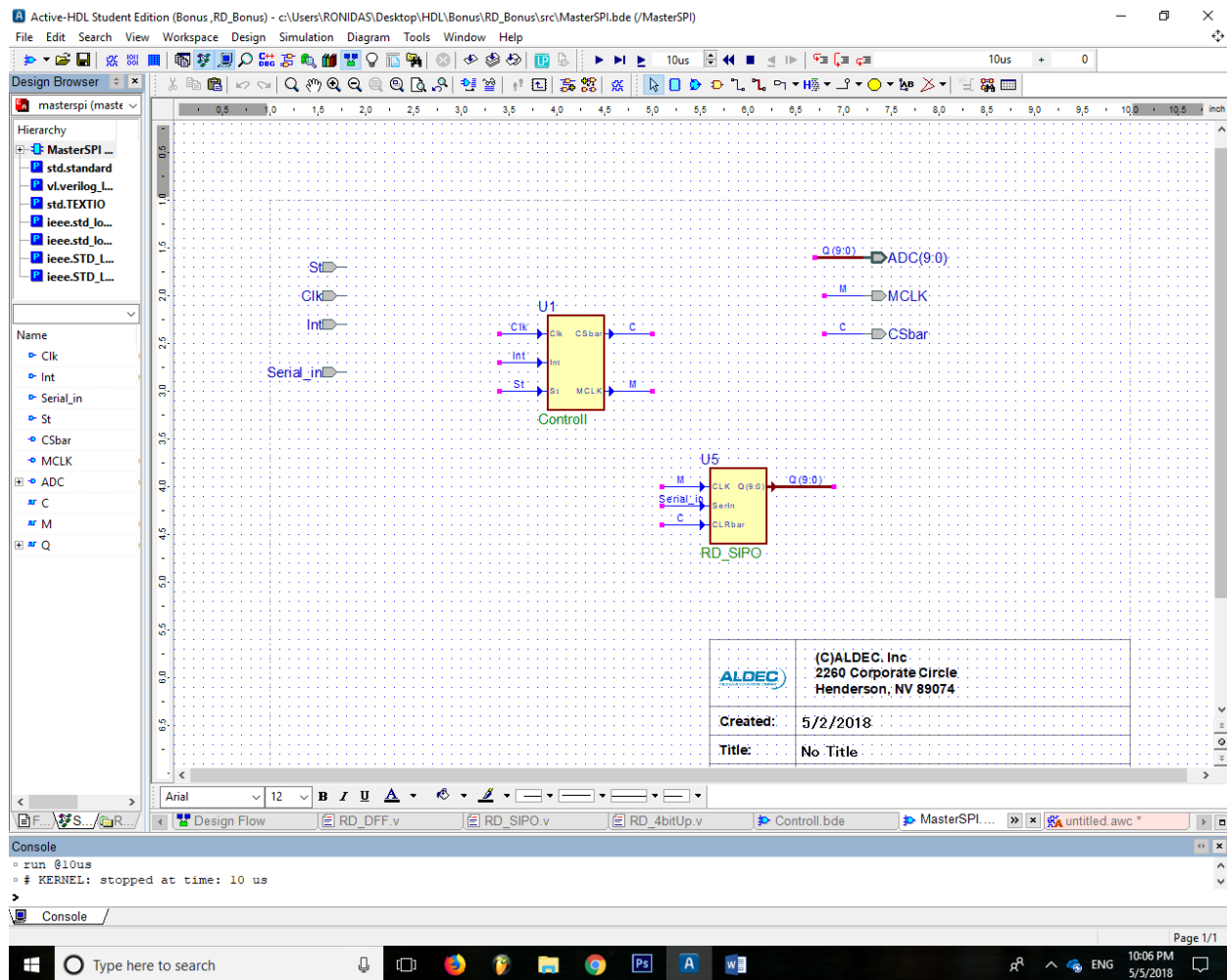


Figure 11 : Schematic for Master SPI for communication with 10-bit ADC.

4-bit up Counter is situated inside the unit “Control” (described in Figure 9). SIPO takes in data from ADC output and show us the results in parallel . For simulation purposes Serial\_in was set to 1.

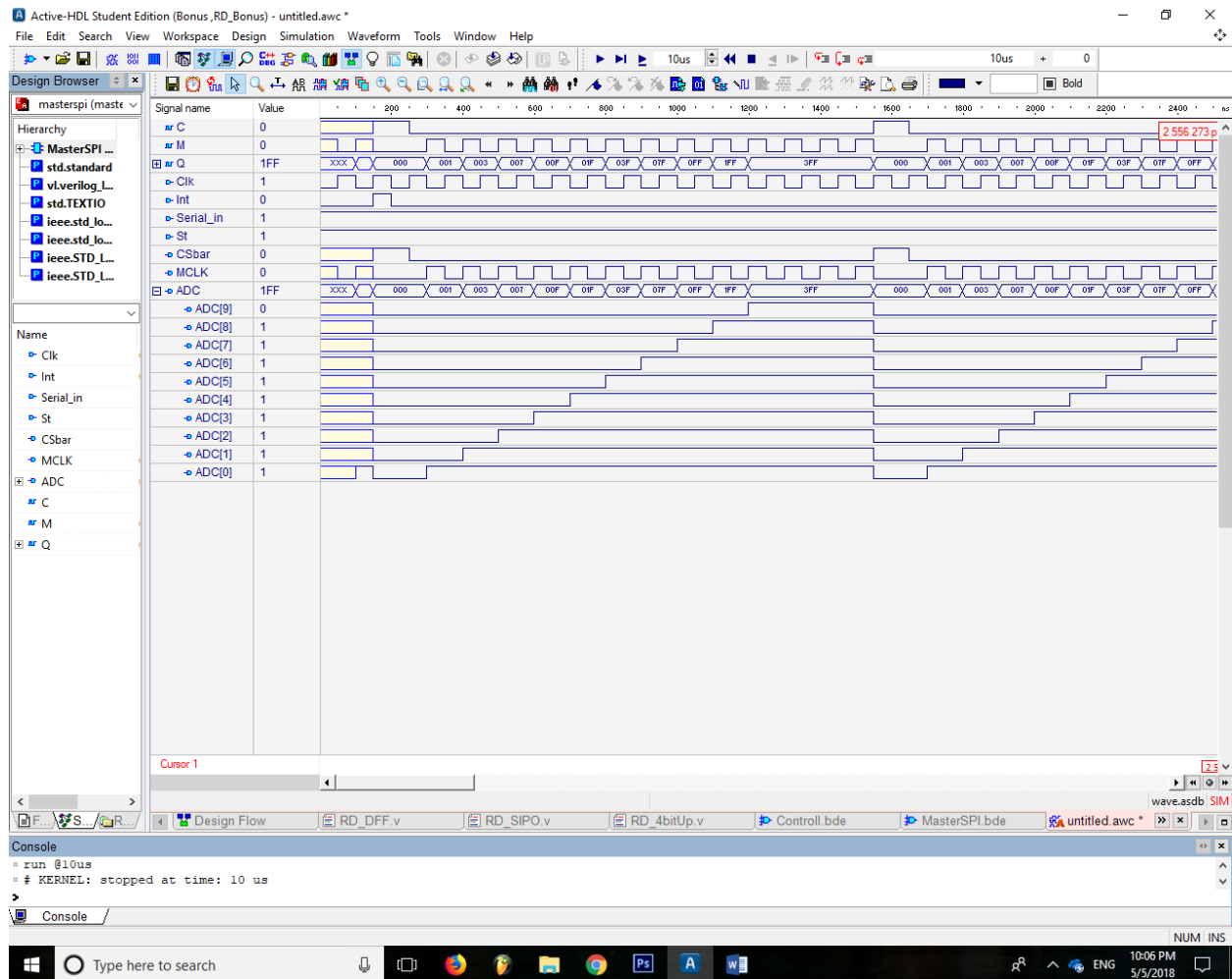


Figure 12 : Waveforms for Master SPI.

As shown above, all the requirements for communication with ADC MCP3001 is met. The Verilog models and code generated from schematic was processed through IceCube2 for purpose of Bitmap generation. Using the help of Diamond Programmer, FPGA was programmed with Master SPI to communicated with 10-bit ADC MCP3001. Pin layouts on FPGA are shown below. Clock was accessed from pin 21 of FPGA device.

<u>J1</u>		<u>J3</u>
<u>Inputs</u>		<u>Outputs</u>
St = 10 → 119		MCLK = 87
Ent = 8 → 117		CSbar = 88
<del>#</del> Sin = 6 → 115		D9 = 44
		D8 = 45
		D7 = 47
		D6 = 48
		D5 = 56
		D4 = 60
		D3 = 61
		D2 = 62
		D1 = 78
		D0 = 79

Figure 13: Pin layouts selected using IceCube2.

Clock was accessed from pin 21 of FPGA device. Therefore, no external clock was applied to the system .


 


Figure 14 : Experimental set-up for the System.

 

Once again, datasheet of MCP3001 was used as reference and pins were connected appropriately. Due to limited availability of logical probes from MSO-19, Bit : D9 – D5 was captured on the screen ( 5 MSB). Last two probes were used to monitor CSbar and Clock applied to ADC. Probe 1 from MSO-19 provided Initiation for the circuit. ADC was powered and grounded from FPGA unit. Data and Results follows below.



## Data and results:

Vref = 3.3 V

IN+ = 3.3 V

IN- = GND



Figure 15: Waveforms obtained ADC for Vref = 3.3 V and Vin = 3.3 (approx.)

With 10-bit resolution ADC, max voltage converts to decimal value = 1024; +/- 1 LSB in each tier of DC value. Using, we can calculated expected Digital output of when Vin = 3.3 V.

$$\text{Digital Output Code} = \frac{1024 * V_{IN}}{V_{REF}}$$

$$\text{Digital Output Code} = \frac{1024 * 3.3V}{3.3V} = 1024$$

Above results D9-D5 = 1 on last clock periods just before CSbar = 1 ; correspond decimal 1023 if we consider +1 LSB for D9 output.

$V_{ref} = 3.3 \text{ V}$   
 $IN+ = 1.61 \text{ V}$   
 $IN- = \text{GND}$

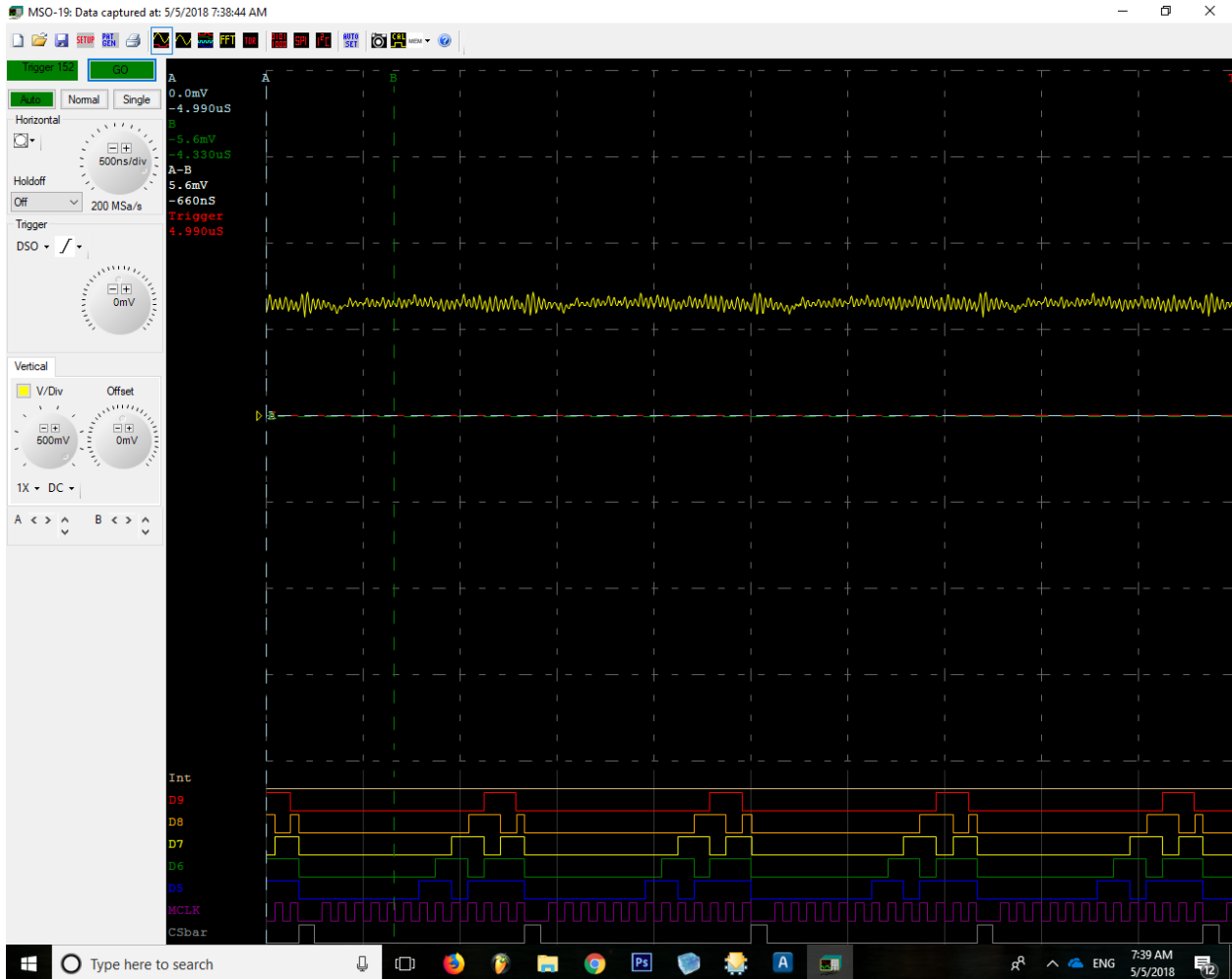


Figure 16 : Output waveforms for ADC for  $V_{ref} = 3.3 \text{ V}$  ;  $V_{in} = 1.61 \text{ V}$ . (MSB : D9-D5 shown)

Using Voltage division, by using two resistors of 10K each, an intermediate voltage was obtained at  $IN+$  node of MCP3001.  $IN-$  node (pin 3) of ADC was ground for an accurate conversion. Noise from  $IN-$  subtracts from  $IN+$  to provide  $V_{in}$ . However, we can approximate conversion using.

$$\text{Digital Output Code} = \frac{1024 * V_{IN}}{V_{REF}}$$

$$\text{Digital Output Code} = \frac{1024 * 1.61V}{3.3V} = 499 ; \quad \text{Bin} = 0111110011 ;$$

Vref = 3.3 V  
 IN+ = GND  
 IN- = GND

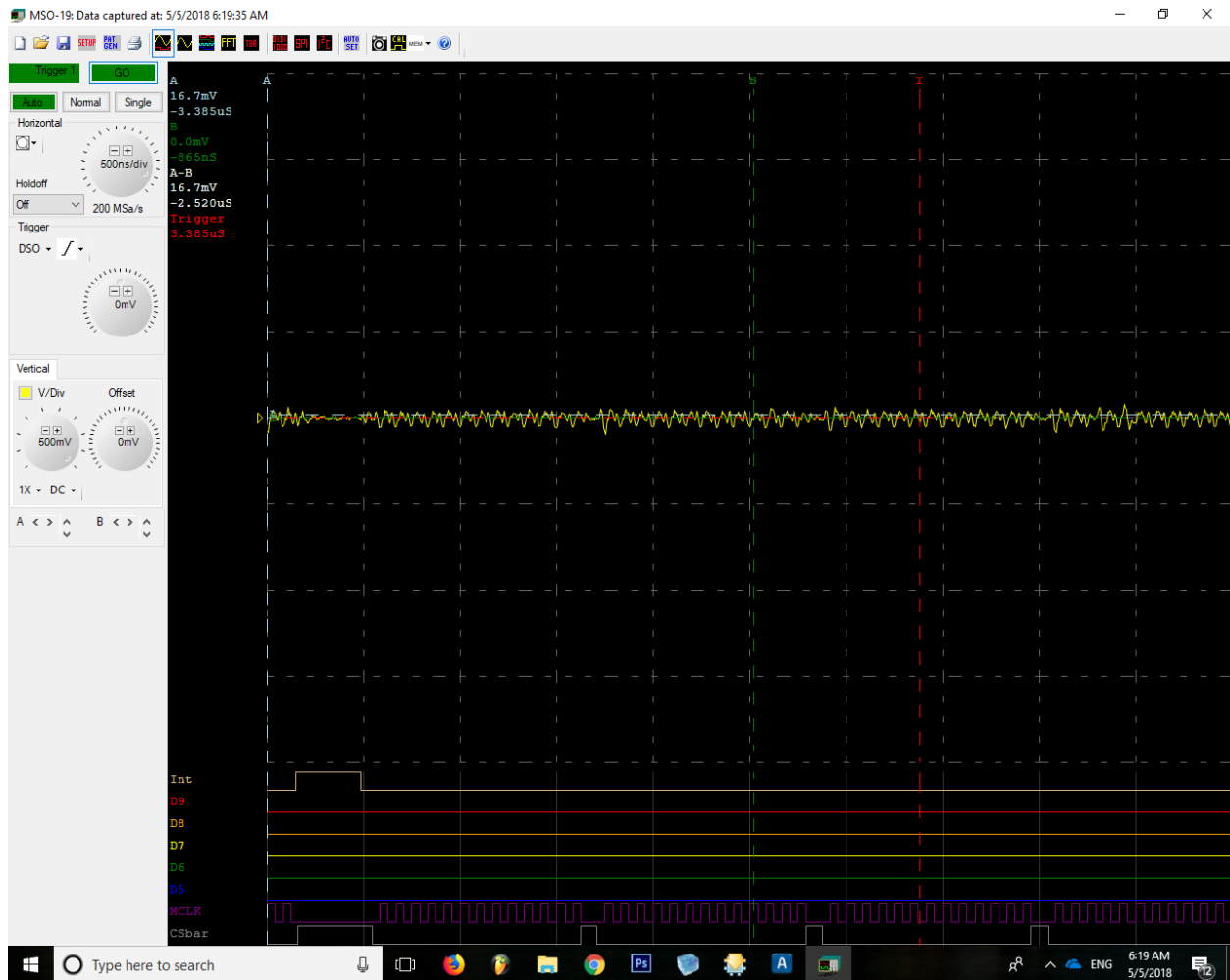


Figure 17 : Output waveforms for ADC for Vref= 3.3 V ; Vin= 0V(approx.).(MSB : D9-D5 shown)

$$\text{Digital Output Code} = \frac{1024 \times 0V}{3.3V} = 0$$

As expected differential voltage between IN+ and IN- is very close to 0. Therefore, Digital output code for Analog value of 0 V is 0 (from D9-D0).

**Conclusion :** Design the Master controller based on IceStick FPGA with SPI-compatible protocol for communication with 10-bit ADC MCP3001 was carried out in this laboratory experiment. Using the knowledge of HDL an FPGA was programmed to carry out all operations to reach objective successfully. ADC paves a meaningful way for processing information in today's digital realm.